



Design with Operational Amplifiers and Analog Integrated Circuits – 4th Edition

Sergio Franco
San Francisco State University

McGraw-Hill Education, ©2015 - ISBN 0-07-232084-2

Contents

Preface xi

1 Operational Amplifier Fundamentals 1

- 1.1 Amplifier Fundamentals 3
- 1.2 The Operational Amplifier 6
- 1.3 Basic Op Amp Configurations 9
- 1.4 Ideal Op Amp Circuit Analysis 16
- 1.5 Negative Feedback 24
- 1.6 Feedback in Op Amp Circuits 30
- 1.7 The Return Ratio and Blackman's Formula 38
- 1.8 Op Amp Powering 46
 - Problems 52
 - References 65
 - Appendix 1A Standard Resistance Values 65

2 Circuits with Resistive Feedback 67

- 2.1 Current-to-Voltage Converters 68
- 2.2 Voltage-to-Current Converters 71
- 2.3 Current Amplifiers 79
- 2.4 Difference Amplifiers 80
- 2.5 Instrumentation Amplifiers 87
- 2.6 Instrumentation Applications 93
- 2.7 Transducer Bridge Amplifiers 99
 - Problems 105
 - References 113

3 Active Filters: Part I 114

- 3.1 The Transfer Function 118
- 3.2 First-Order Active Filters 123
- 3.3 Audio Filter Applications 130
- 3.4 Standard Second-Order Responses 135
- 3.5 KRC Filters 142
- 3.6 Multiple-Feedback Filters 149
- 3.7 State-Variable and Biquad Filters 154
- 3.8 Sensitivity 160

Problems 163
References 170

4 Active Filters: Part II 171

- 4.1 Filter Approximations 172
- 4.2 Cascade Design 178
- 4.3 Generalized Impedance Converters 185
- 4.4 Direct Design 191
- 4.5 The Switched Capacitor 197
- 4.6 Switched-Capacitor Filters 202
- 4.7 Universal SC Filters 208
 - Problems 214
 - References 220

5 Static Op Amp Limitations 221

- 5.1 Simplified Op Amp Circuit Diagrams 223
- 5.2 Input Bias and Offset Currents 229
- 5.3 Low-Input-Bias-Current Op Amps 234
- 5.4 Input Offset Voltage 238
- 5.5 Low-Input-Offset-Voltage Op Amps 243
- 5.6 Input Offset Error and Compensation Techniques 248
- 5.7 Input Voltage Range/Output Voltage Swing 253
- 5.8 Maximum Ratings 259
 - Problems 261
 - References 267
 - Appendix 5A Data Sheets of the μ A741 Op Amp 268

6 Dynamic Op Amp Limitations 277

- 6.1 Open-Loop Frequency Response 278
- 6.2 Closed-Loop Frequency Response 283
- 6.3 Input and Output Impedances 290
- 6.4 Transient Response 294
- 6.5 Effect of Finite GBP on Integrator Circuits 301
- 6.6 Effect of Finite GBP on Filters 310
- 6.7 Current-Feedback Amplifiers 315
 - Problems 324
 - References 331

7 Noise 333

- 7.1 Noise Properties 335
- 7.2 Noise Dynamics 340
- 7.3 Sources of Noise 344
- 7.4 Op Amp Noise 350
- 7.5 Noise in Photodiode Amplifiers 357
- 7.6 Low-Noise Op Amps 361
 - Problems 365
 - References 369

8 Stability 371

- 8.1 The Stability Problem 372
- 8.2 Phase and Gain Margin Measurements 382

- 8.3 Frequency Compensation of Op Amps 388
- 8.4 Op Amps Circuits with a Feedback Pole 400
- 8.5 Input-Lag and Feedback-Lead Compensation 409
- 8.6 Stability in CFA Circuits 414
- 8.7 Composite Amplifiers 418
 - Problems 423
 - References 433

9 Nonlinear Circuits 434

- 9.1 Voltage Comparators 435
- 9.2 Comparator Applications 443
- 9.3 Schmitt Triggers 450
- 9.4 Precision Rectifiers 456
- 9.5 Analog Switches 462
- 9.6 Peak Detectors 467
- 9.7 Sample-and-Hold Amplifiers 471
 - Problems 477
 - References 482

10 Signal Generators 483

- 10.1 Sine Wave Generators 485
- 10.2 Multivibrators 491
- 10.3 Monolithic Timers 499
- 10.4 Triangular Wave Generators 505
- 10.5 Sawtooth Wave Generators 510
- 10.6 Monolithic Waveform Generators 512
- 10.7 V - F and F - V Converters 520
 - Problems 526
 - References 532

11 Voltage References and Regulators 534

- 11.1 Performance Specifications 536
- 11.2 Voltage References 541
- 11.3 Voltage-Reference Applications 548
- 11.4 Linear Regulators 553
- 11.5 Linear-Regulator Applications 558
- 11.6 Switching Regulators 566
- 11.7 The Error Amplifier 574
- 11.8 Voltage Mode Control 577
- 11.9 Peak Current Mode Control 582
- 11.10 PCMC of Boost Converters 594
 - Problems 600
 - References 607

12 D-A and A-D Converters 608

- 12.1 Performance Specifications 610
- 12.2 D-A Conversion Techniques 616
- 12.3 Multiplying DAC Applications 629
- 12.4 A-D Conversion Techniques 634
- 12.5 Oversampling Converters 644
 - Problems 652

References 655

13 Nonlinear Amplifiers and Phase-Locked Loops 657

13.1 Log/Antilog Amplifiers 658

13.2 Analog Multipliers 665

13.3 Operational Transconductance Amplifiers 670

13.4 Phase-Locked Loops 678

13.5 Monolithic PLLS 686

Problems 693

References 696